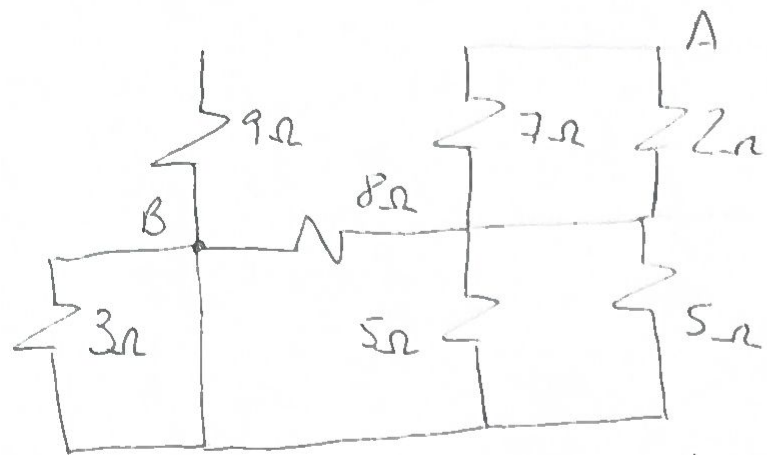



OCTUBRE 2025

1. Pasivamos fuente, bobina y condensador

$$R_{th} = (7//2) + (8//5//5) = 3,46\Omega$$



Planteamos el sistema por ruidos

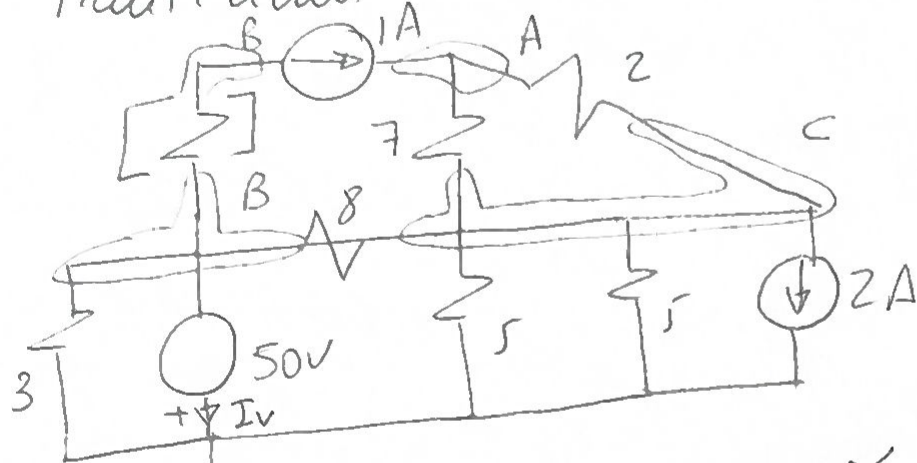


$$\begin{pmatrix} 1/2 + 1/7 & 0 & -1/2 - 1/7 \\ 0 & 1/3 + 1/8 & -1/8 \\ -1/2 - 1/7 & -1/8 & 1/8 + 1/2 + 1/5 + 1/5 + 1/3 \end{pmatrix} \begin{pmatrix} V_A \\ V_B \\ V_C \end{pmatrix} = \begin{pmatrix} 1 \\ -1 - I_v \\ -2 \end{pmatrix}$$

$$0 - V_B = 50$$

4 ecuaciones  
4 incógnitas

Resolvemos por superposición.

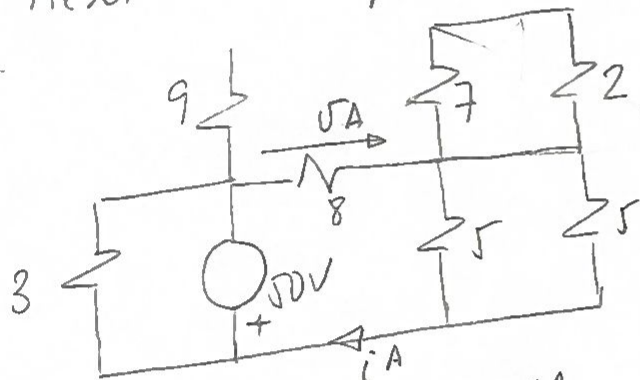


$$i^A = -\frac{50}{8+2,5} = -4,76A$$

$$V^A = -50 \frac{8}{8+2,5} = -38,09V$$


$$i = i^A + i^B + i^C = -3,524A$$

$$V = V^A + V^B + V^C = -36,185V$$

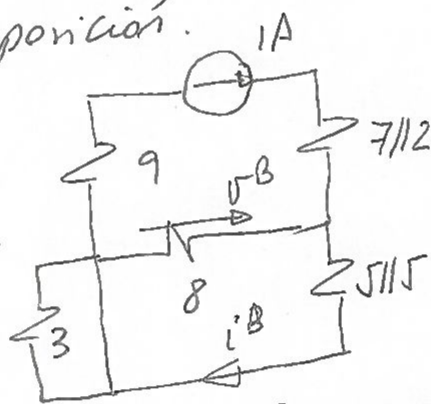


$$i^B = 1 \frac{8}{8+2,5} = 0,76A$$

$$V^B = -8 \frac{2,5}{8+2,5} = -1,904V$$

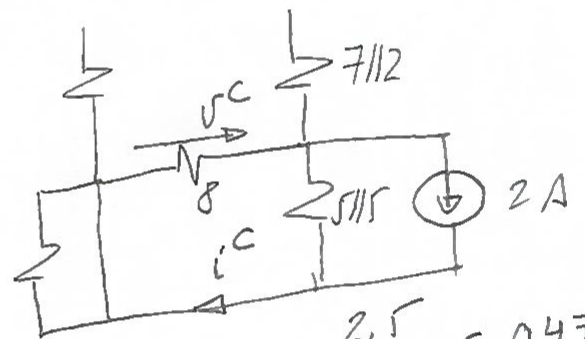

$$i^C = 2 \frac{2,5}{8+2,5} = 0,476A$$

$$V^C = 8 i^C = 3,809V$$

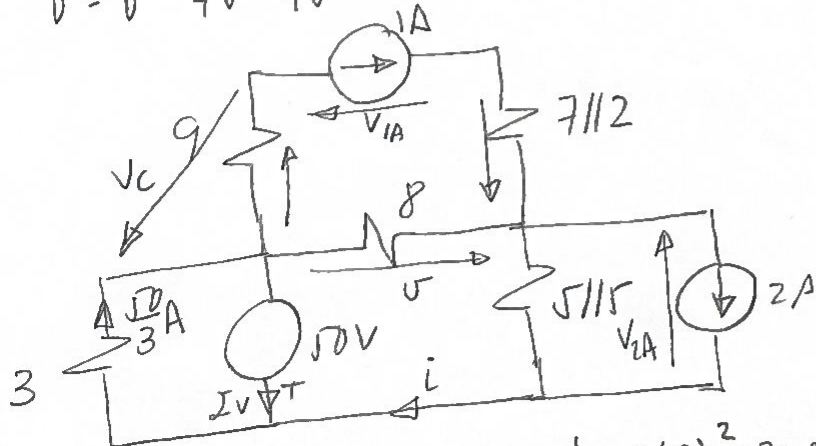

$$V_C = 9 \cdot 1 = 9V \quad E_C = \frac{1}{2} 9 \cdot 5 (1)^2 = 20,25J$$

$$E_L = \frac{1}{2} 1 \cdot 2 (-3,524)^2 \Rightarrow E_L = 7,45J$$

$$I_v + i = \frac{50}{3} \Rightarrow I_v = \frac{50}{3} - i = 20,9A$$

$$P_{50V} = 50 \cdot 20,9 = 1045,53W \text{ (generada)}$$


$$V_{2A} = 50 + V \Rightarrow V_{2A} = 13,815V$$

$$P_{2A} = 2 \cdot V_{2A} = 27,63W \text{ (generada)}$$

$$V_{1A} = (7//2) \cdot 1 - 5 + 9 \cdot 1 = 46,74V$$

$$P_{1A} = 1 \cdot V_{1A} = 46,74W \text{ (generada)}$$

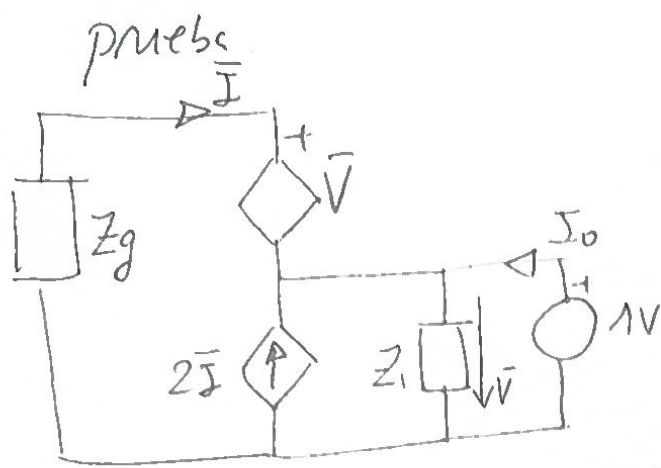3. Calculamos la  $Z_{th}$  con el método de fuente de



$$\bar{V} = 1$$

$$\bar{V} + 1 + \bar{Z}_g \bar{I} = 0 \Rightarrow \bar{I} = -2/\bar{Z}_g$$


$$\bar{I}_0 + \bar{I} + 2\bar{I} = \frac{1}{\bar{Z}_1} \Rightarrow \bar{I}_0 = \frac{1}{\bar{Z}_1} + \frac{6}{\bar{Z}_g}$$

$$\bar{I}_0 = 0,02 - 0,072j \quad Z_{th} = \frac{1}{\bar{I}_0} \Rightarrow Z_{th} = 3,6 + 12,8j$$

Por lo tanto  $Z^{max} = Z_{th}^* \Rightarrow Z^{max} = 3,6 - 12,8j$

$R = 3,6 \Omega \quad L = 0 \quad C = 248,67 \mu F$

Calculamos la  $V_{th}$

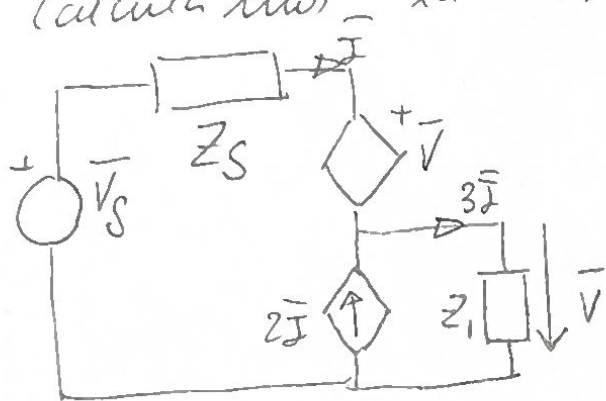

$$\bar{V} = 3\bar{I} \bar{Z}_1$$

$$\bar{V}_g = \bar{Z}_g \bar{I} + 2\bar{V} \Rightarrow \bar{V}_g = \bar{Z}_g \bar{I} + 6\bar{Z}_1 \bar{I} \Rightarrow$$

$$\Rightarrow \bar{I} = \frac{\bar{V}_g}{\bar{Z}_g + 6\bar{Z}_1} \Rightarrow \bar{I} = 0,02 - 0,04j$$

$$\bar{V} = 7,8 - 0,6j \quad \bar{V}_{th} = 7,8 - 0,6j$$


$$\hat{I} = \frac{V_{th}}{Z_{th} + Z^{max}}$$

$$\frac{7,8 - 0,6j}{2 \cdot 3,6} = 1,0833 - 0,0833j = 1,086 \angle -4,4^\circ$$

$$P = 3,6 \cdot (1,086)^2 = 4,25W$$

$$Q = -12,8 (1,086)^2 = -15,11VAR$$

4. Resolvamos el circuito

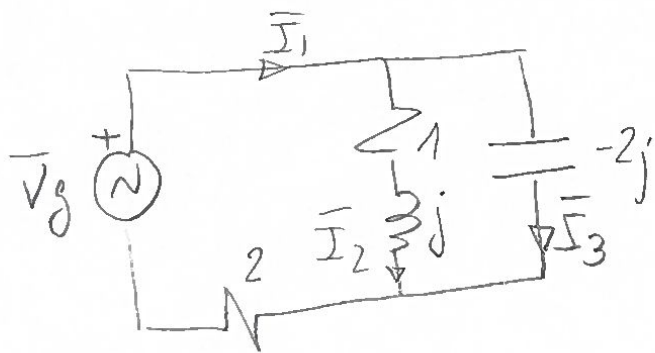

$$\bar{I}_1 = \frac{\bar{V}_g}{2 + (-2j) \parallel (1+j)} = 5A \Rightarrow \boxed{A_1 = 5A}$$

$$\bar{I}_2 = \bar{I}_1 \frac{-2j}{-2j + 1 + j} = 5 - 5j \Rightarrow \boxed{A_2 = 7,07A}$$

$$\bar{I}_3 = \bar{I}_1 - \bar{I}_2 = 5 - 5 + 5j = 5j \Rightarrow \boxed{A_3 = 5A}$$

$$P_g = 20 \cdot 5 = 100W$$

$$Q_g = 0 VAR$$

2. Ejercicio resuelto en el examen de Junio 2024