PARCIAL ENERO 2025 $I_3 = 10\sqrt{3} \ D_3 = 10\sqrt{3} \ D_3$ $\frac{S_2(hifásia) = 1W + 4Wj}{S_2(monohísia)} = \frac{1W}{3} + \frac{4W}{3}J VA$ $\frac{S_2(mon) = \frac{1VI^2}{2z^*} \Rightarrow z_2 = \frac{3(139,64)^2}{1W - 4Wj} \Rightarrow z_2 = \frac{34,41 + 137,64j}{2z^*} S2$ $I_3 = I_1 \frac{Z_2}{Z_2 + Z_3 + \frac{Z_4}{3}} =)I_1 = \frac{I_3 (Z_2 + Z_3 + \frac{Z_4}{3})}{Z_2} = 18,27 - 0,27jA = 18,27 - 0.84A$ $V_{g} = \overline{Z}_{1}\overline{Z}_{1} + \overline{V} = (1+2_{j})18,27[-0,89] + 139,69[60,21] = 180,46[60,78] V$ A = 18,27A V, = 312,56V V2 = 241,86V $Zeq = Z_1 + (Z_2)/(Z_3 + Z_4/3) = 4,69 + 8,69$. Yeq = 0,0481 - 0,08907(UC= 0,08907 => C1 = 283,51 mF. [C4 = 94,506 mF] Semennia directa porque W270 y le carge es induction · ESERCICIO 2 [W4 = W1 = 500W.] Pc = 3W1 = 1500 W. Qc = 1732,05 var. Coloco Ws en fase 5 tal que W3 y Ws for mon método 2 vatimetros W3+ W5 = 1500 => W5 = 1520 - W3 $(W_3 - W_5)V_3 = 1732,05 \Rightarrow (2W_3 - 15w)V_3 = 1732,05 \Rightarrow |W_3 = 1250w|$ EJERCICIO 3 | |VLI /V3 = 3,464 | Módulo de 2: |Z| = |JLI| Z = 3964 [23,17°_12 Angulo de 2: W= |VL|. |IL|. (Os(0+30) => 0=22,17° Cuando el interruptor se abre: $\bar{J} = \frac{150[30^{\circ}]}{2.7} = 21,67[57.17^{\circ}] \rightarrow [A=21,67A]$ [V=150V]

W= 150-21,67. cos (-30-52,17) => W= 442,83 W]