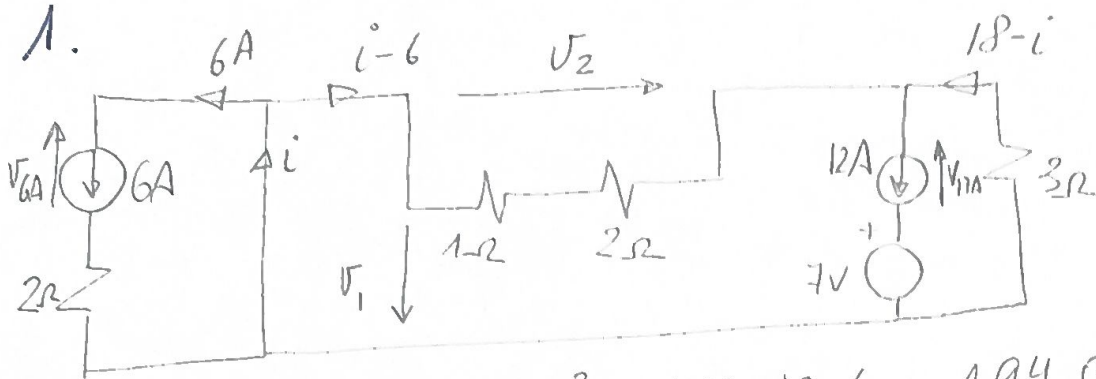


1.



$$3(i-6) - 3(18-i) = 0 \Rightarrow$$

$$\Rightarrow 6i = 3 \cdot (18+6) \Rightarrow i = 12A$$

$$M = K \sqrt{L_1 L_2} = 1,202mH$$

$$E_L = \frac{1}{2} 1i^2 + \frac{1}{2} 2(6)^2 + 1,202 \cdot 12 \cdot 6 = 194,544mJ$$

$$V_1 = 0 \Rightarrow E_{C1} = 0J \quad V_2 = 3 \cdot 6 = 18V \quad E_{C2} = \frac{1}{2} 2(18)^2 = 324mJ$$

$$E_T = 518,544mJ$$

$$V_{6A} = 12V \quad P_{6A} = 12 \cdot 6 = 72W (gen)$$

$$P_{7V} = 7 \cdot 12 = 84W (con)$$

$$V_{12A} = 7 + 3(18-i) = 25V \quad P_{12A} = 12 \cdot 25 = 300W (gen)$$

$$V_{AB} = -3(18-i) - 5(1,5i) = -108V$$

2.

$$P_L = 3 \cdot 1 \cdot (24,5)^2 = 1800,75W$$

$$Q_L = 3 \cdot 3 \cdot (24,5)^2 = 5402,25VAR$$

$$P_C = P_T - P_L = 9003,75W$$

$$Q_C = Q_T - Q_L = 9004,08VAR$$

$$S_C = \sqrt{P_C^2 + Q_C^2} = 12733,46VA = \sqrt{3} \cdot |V_2| \cdot 24,5 \Rightarrow |V_2| = 300,06V$$

$$S_T = \sqrt{P_T^2 + Q_T^2} = 18007,76VA = \sqrt{3} \cdot |V_1| \cdot 24,5 \Rightarrow |V_1| = 424,35V$$


$$C^A = \frac{P_C \cdot (\cos \phi_C - 1)}{2\pi f |V_2|^2} = \frac{9004,08}{2\pi 50 (300,06)^2} = 318,32\mu F \quad C^A = 106,108\mu F$$

Después de conectar el condensador.
la carga consume 9003,75W a una tensión 300,06V, por lo tanto


$$\frac{9003,75}{Z'} = \frac{(300,06/\sqrt{3})^2}{R^A} \Rightarrow R^A = 10\Omega$$

$$\bar{I} = \frac{424,35/\sqrt{3}}{1 + 3j + 10} = 21,48 \angle -15,25^\circ \Rightarrow A_1' = 21,48A$$
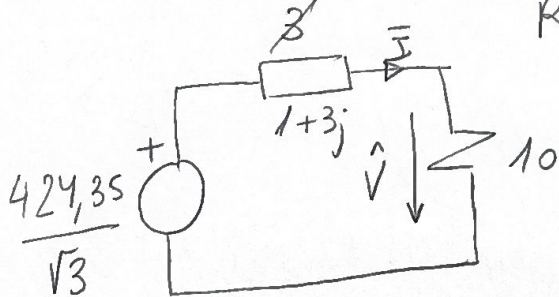
$$\hat{V} = 10 \cdot \bar{I} = 214,8 \angle -15,25^\circ \quad V_2' = \sqrt{3} \cdot 214,8 = 372,17V$$



3.

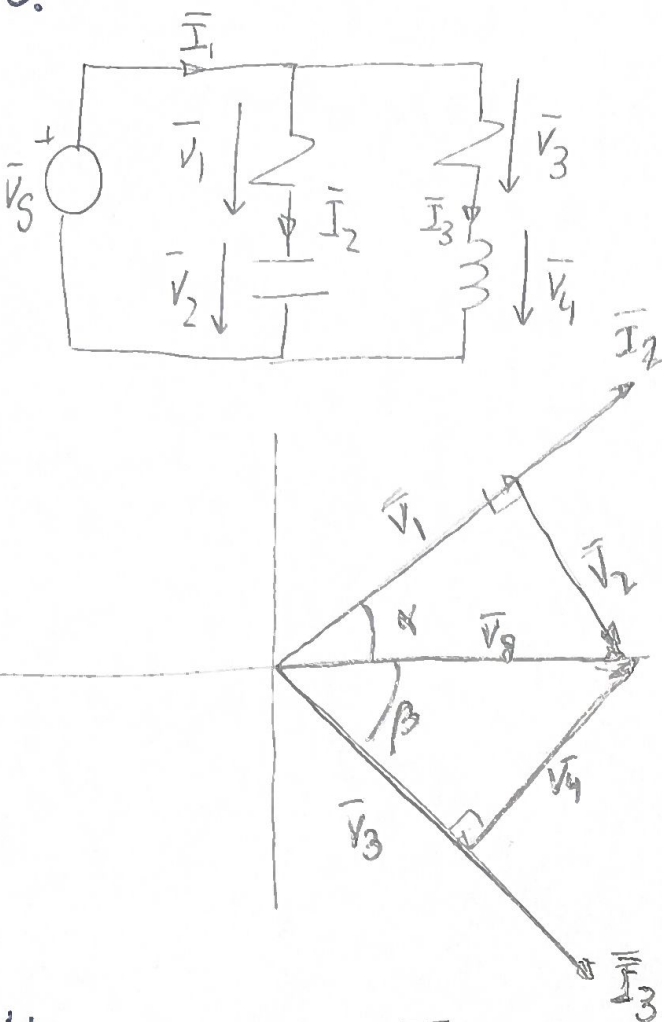

$$|V_S| = \sqrt{|V_1|^2 + |V_2|^2} = 125V$$

$$|V_4| = \sqrt{|V_5|^2 - |V_3|^2} = 100 \text{ V}$$

$$\alpha = \arctan \frac{|V_2|}{|V_1|} = 73,74^\circ$$

$$\beta = \arctg \frac{|V_4|}{|V_3|} = 53,13^\circ$$

$$\bar{I}_1 = 5 \underline{173,74} + 3 \underline{-153,13} = 4 \underline{36,87} \text{ A}$$

$$|I_1| = 4 \text{ A.}$$

$$|I_1| = 4 \text{ A.}$$

$$\bar{S}_g = \bar{V}_s \bar{I}_1^* = 125 \angle 0^\circ 4 \angle -36.87^\circ = 400 - 300j \quad \left. \begin{array}{l} \text{generate } 400 \text{ W} \\ \text{consume } 300 \text{ W} \end{array} \right\}$$

P_{av} = 400 W

$$\vec{S}_I = 9W - 4Wj = \hat{V} \cdot \vec{I}_g^* \Rightarrow \hat{V} = \frac{9W - 4Wj}{10} = 90 - 40j$$

$$\bar{J}_S = 10 \text{ L}^\circ$$

$$\begin{aligned} \begin{pmatrix} 5 & -2j & -5 \\ -2j & 1+j & j \\ -5 & j & 6-j \end{pmatrix} \begin{pmatrix} \bar{I}_a \\ \bar{I}_b \\ \bar{I}_c \end{pmatrix} &= \begin{pmatrix} -90+40j \\ \bar{V}_S \\ 90-40j \end{pmatrix} \quad (1) \\ & \quad (2) \\ & \quad (3) \end{aligned}$$

$$\bar{I}_C - \bar{I}_A = 10 \Rightarrow \bar{I}_C = 10 + \bar{I}_A$$

$$\bar{I}_C - I_a = 10 \Rightarrow \bar{I}_C = 10 + 40j \Rightarrow \bar{I}_b = -20 - 20j$$

$$(1) \rightarrow 5\bar{I}_a - 2j\bar{I}_b - 5(\bar{I}_a + 10) = -90 + 40j \Rightarrow -2j\bar{I}_b = -40 + 10j$$

$$(1) \rightarrow 5\bar{I}_a - 2j\bar{I}_b - 5(10 + \bar{I}_a) = -10 + 10j \Rightarrow \bar{I}_c = 20 \angle 0^\circ$$


$$(3) \rightarrow -5\bar{I}_a + j\bar{I}_b + (6-j)(10 + \bar{I}_a) = 90 + 40j \Rightarrow \bar{I}_a = 10 \angle 0^\circ$$

$$(2) \rightarrow 2\bar{I}_a - 2\bar{I}_b = -40j \Rightarrow \bar{I}_b = -40j = 40 \angle -90^\circ \Rightarrow \begin{cases} v = 40V \\ i = -90^\circ \end{cases}$$

$$(2) \rightarrow \bar{V}_S = -2j(10) + (1+j)(-20-20j) + j20 \Rightarrow \bar{V}_S = -40j = 40 \angle -90^\circ \Rightarrow \begin{cases} V = 40 \text{ V} \\ \phi = -90^\circ \end{cases}$$


$$\overline{S}_r = \overline{V}_s \cdot \overline{I}_b^* = -40j (20 + 20j) = 800 + 800j \quad \left\{ \begin{array}{l} \text{generasi sumber} \\ \text{generasi sumber} \end{array} \right.$$

Pasivamos fuentes y calculamos I_{th}

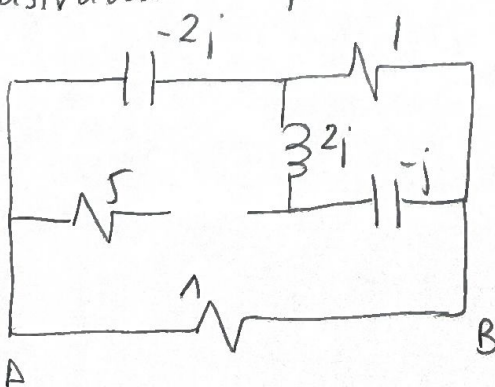

$$z_{th} = [(2j - j) // 1 - 2j] // 1 = 0,667 - 0,33j$$

$$R^{\max} = |Z_{th}| = 0,745 \Omega \quad V_{th} = 1 \cdot \bar{I}_C = 20 \angle 0^\circ V$$


 $P^{\max} = 0,745 \cdot (13,79)^2 = 141,72 \text{ W}$